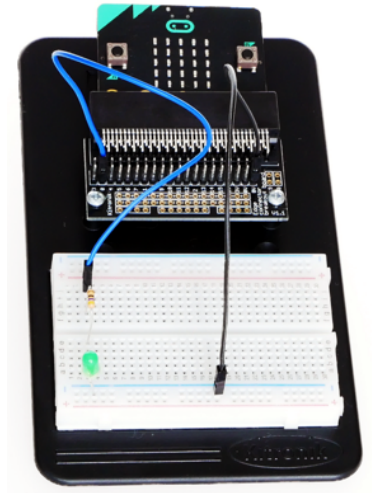


Flashing LED

Goal: Set-up of a flash circuit

Content: LED, series resistor, Ohm's law, digital output, pauses



LESSON 1


Assignment

Using the Micro Bit and the components of the Inventor's Kit, a flash circuit is to be set up. One LED of your choice should flash every second.

Ingredients

Components + cable



Breadboard

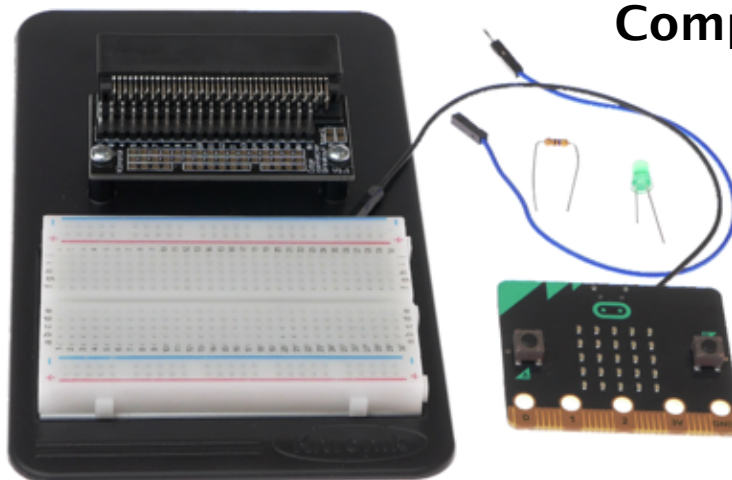

Microbit

LESSON 2

Circuit set-up

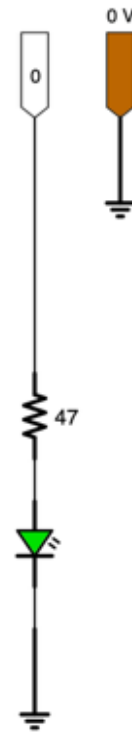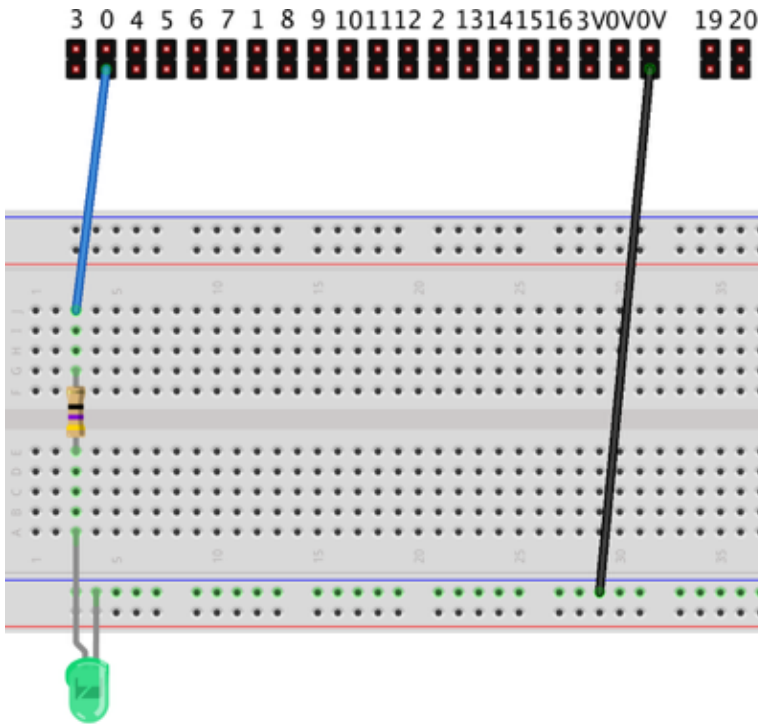

- Position the LED as illustrated. The long pin (anode) faces upwards to the series resistor.
- The short pin (cathode) is routed to the common Gnd (- pole).
- The long pin is routed via a series resistor (47 Ohm) to the output pin of the Micro Bit. [Blue cable - Pin0]
- In the end, the ground bar (Gnd - 0V) is connected to the Micro Bit. [Black cable - 0V]

Info

Detailed information on the term "**series resistor**" will be the topic of other lessons.

LESSON 3

Block code of the flashing LED



```
dauerhaft
schreibe digitalen Wert von Pin P0 auf 1
pausiere (ms) 500
schreibe digitalen Wert von Pin P0 auf 0
pausiere (ms) 500
```

The image shows a Scratch code block for a loop labeled 'dauerhaft'. It contains four blocks: a red 'schreibe digitalen Wert von Pin P0 auf 1' block, a blue 'pausiere (ms) 500' block, a red 'schreibe digitalen Wert von Pin P0 auf 0' block, and another blue 'pausiere (ms) 500' block.

Information on block code

```
dauerhaft
schreibe digitalen Wert von Pin P0 auf 1
  pausiere (ms) 500
schreibe digitalen Wert von Pin P0 auf 0
  pausiere (ms) 500
```

The "permanently" loop ensures that all blocks (commands) in a program are "infinitely" executed.

In the beginning, the LED (connected to pin 0) is activated.

The pause specifies the flashing frequency (the speed of flashing of the LED).

Afterwards, the LED is deactivated again

Even after the LED is activated, a respective pause is required.

LESSON 4

optional: Calculation of series resistors of LEDs

Ohm's law



$$R = U / I$$

LEDs must not be directly connected to the voltage source as this would destroy it.

Series resistors limit the voltage as well as the current flow through the LED.

The admissible voltage and current rating of the LED can be found in the data sheet.

Example

Voltage source: 5V

LED: $U = 2V$
 $I = 20mA$

The voltage, which has to "get rid of", is converted into heat $\Rightarrow 5V - 2V = 3V$

$$R[\text{Ohm}] = U[\text{V}] / I[\text{A}]$$

$$R = 3 / 0,02 = 300 / 2 = 150$$